

Test in Class -----Chapter1-4

1. Add the two BCD numbers: 1000 0011 and 0010 0101. (0001 0000 1000)
2. Convert the Gray code 1011 0101 to binary. (1101 1001)
3. An odd parity system receives the following code groups: 1001 0100, 1000 1000, and 1101 0001. Determine which groups, if any, are in error. (10001000,11010001)
4. A basic 2-input logic circuit has a HIGH on one input and a LOW on the other input, and the output is HIGH. What type of logic circuit is it?
(An OR gate or an exclusive-OR gate)
5. Write the output expression for the circuit in Figure 1 in SOP form. ($A \bar{B} \bar{C} \bar{E} + A \bar{B} \bar{D} \bar{E}$)

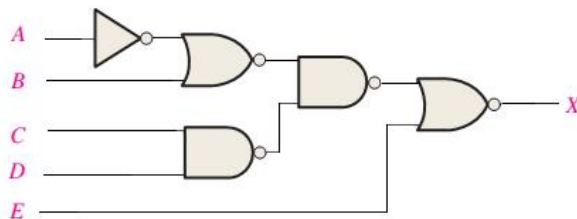


Figure 1

6. Write the output expression for a circuit with input waveform and output waveform, as shown in Figure 2. ($AB + \bar{A} \bar{B}$)

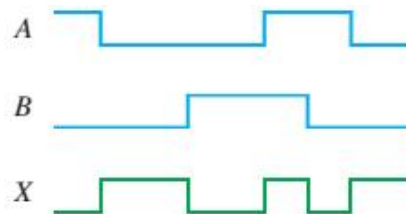


Figure 2

7. Figure 3 shows a (D) diagram.
(A) circuit (B) logic (C) state (D) timing

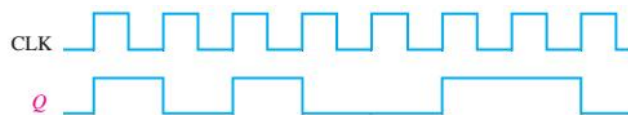


Figure 3

8. The signed number -101_2 is expressed as a 4-bit number 1011_2 in the (C) form.
(A) sign-magnitude (B) 1's complement (C) 2's complement (D) offset binary
9. The 2's complement number system can represent integers in the range (B), where n is the number of bits available for the representation.

- (A) $0 \leq N \leq 2^n - 1$ (B) $-2^{n-1} \leq N \leq 2^{n-1} - 1$ (C) $-2^n \leq N \leq 2^n - 1$ (D) None of the above

10. A periodic waveform has frequency of 100Hz and a pulse width of 0.05ms. The duty cycle is (A)

- (A) 0.5% (B) 5% (C) 50% (D) 0.0055%

11. How many of the following statements are false? (C)

- (A) 1 (B) 2 (C) 3 (D) 4

- (1) When a Boolean variable is multiplied by its complement, the result is the variable.
 (2) "The complement of a product of variables is equal to the sum of the complements of each variable" is a statement of DeMorgan's theorem.
 (3) SOP means series of products .
 (4) Karnaugh maps can be used to simplify Boolean expressions.
 (5) A 4-variable Karnaugh map has eight cells.

12. From Figure 4, we can obtain $Y =$ (B)

- (A) $\overline{A}\overline{B}$ (B) $AB + \overline{C}$ (C) $(\overline{A} + \overline{B})C$ (D) None of the above

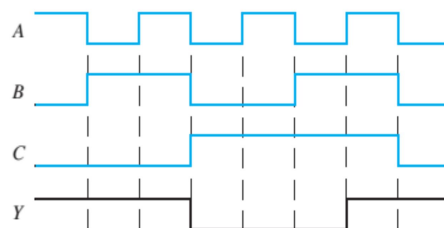


Figure 4

13. The AND operation can be produced with (C) NOR gates.

- (A) 1 (B) 2 (C) 3 (D) None of the above

14. $X = AC + \overline{A}\overline{B} + \overline{A}\overline{C} \neq$ (D)

- (A) $\overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}C + ABC$
 (B) $(A + \overline{B} + \overline{C})(\overline{A} + C)$
 (C) $\overline{A}\overline{C} + \overline{B}C + AC$
 (D) None of the above

15. From the K-map in Figure 5, we obtain the minimum SOP expression: (A)

- (A) $Y = AD + B + \overline{C}\overline{D}$
 (B) $Y = AB + AD + \overline{B}\overline{C}\overline{D}$
 (C) $Y = (A + \overline{D})(B + \overline{C} + D)$
 (D) $Y = (\overline{A} + D)(\overline{B} + C + \overline{D})$

		CD			
		00	01	11	10
AB	00	1	0	X	X
	01	X	X	X	X
	11	1	1	1	1
	10	1	1	1	0

Figure 5

16. The outputs L_1 , L_2 , and L_3 of the 1-bit comparator in Figure 6 indicate (A) respectively.

- (A) $A < B$, $A = B$, and $A > B$
 (B) $A > B$, $A = B$, and $A < B$
 (C) $A < B$, $A \neq B$, and $A > B$
 (D) $A > B$, $A \neq B$, and $A < B$

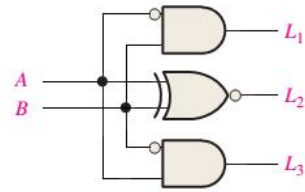


Figure 6

17. The function performed by the circuit in Figure 7 is (A)

- (A) $Y = \bar{A}\bar{B}\bar{C} + \bar{A}BC$ (B) $Y = \bar{A}\bar{B}C + A\bar{B}\bar{C}$ (C) $Y = \bar{A}B\bar{C} + A\bar{B}C$ (D)

$$Y = \bar{A}BC + A\bar{B}\bar{C}$$

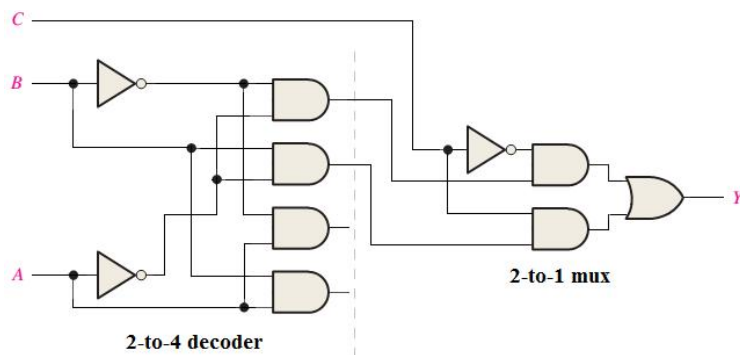


Figure 7

18. Simplify the logic expression.

$$X = \overline{(\bar{A}\bar{B})(\bar{B} + D)(\bar{C}\bar{D})} + BC + \bar{A}(\overline{\bar{B}\bar{D}} + A) + \bar{C}\bar{D} = 1$$

19. Using a Karnaugh map to simplify the following function.

$$F = A\bar{B}\bar{C} + \bar{A}\bar{B} + \bar{A}D + BD + C = \bar{B} + C + D$$